

Lösungen

Aufgabe 1:

- 1.1. $k_1 = 0,72$ $k_2 = 0,28$
- 1.2. $\varphi_1 = 5,56 \text{ V}$ $\varphi_2 = 8,77 \text{ V}$ $\varphi_3 = 20 \text{ V}$
- 1.3. $I = 8,88 \text{ mA}$
 $P = 7,51 \text{ mW}$

Aufgabe 2:

2.1. $D(r) = 259,3 \frac{\text{nAs}}{\text{m}^2} \cdot \frac{1}{\left(\frac{r}{\text{m}}\right)}$ $E(r) = 29,28 \cdot \frac{1 \text{ kV}}{\epsilon_r \text{ m}} \cdot \frac{1}{\left(\frac{r}{\text{m}}\right)}$


$r_3 \leq r \leq r_4$ $\varphi(r) = 14,64 \text{ kV} \cdot \ln\left(\frac{r_4}{r}\right)$

$r_2 \leq r \leq r_3$ $\varphi(r) = \varphi(r_3) = 4,93 \text{ kV}$

$r_1 \leq r \leq r_2$ $\varphi(r) = 4,93 \text{ kV} + 7,32 \text{ kV} \cdot \ln\left(\frac{r_2}{r}\right)$

$r \leq r_1$ $\varphi(r) = U = 10 \text{ kV}$

	$\frac{D}{\text{nAs/m}^2}$	$\frac{E}{\text{kV/m}}$	$\frac{\varphi}{\text{kV}}$
r_2	$6,48 \cdot 10^4$	1830	4,93
r_3	$5,18 \cdot 10^4$	2928	4,93

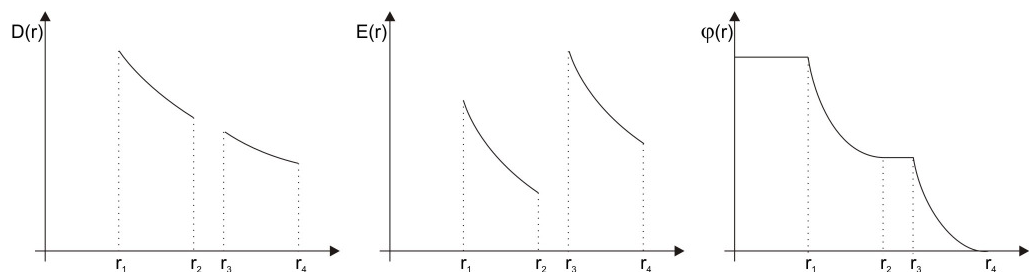


2.2. $U_{p2} = 2,1 \text{ kV}$

Aufgabe 3:

3.1. $f = 62,5 \text{ Hz}$

3.2. $\hat{i} = 0,32 \text{ A}$

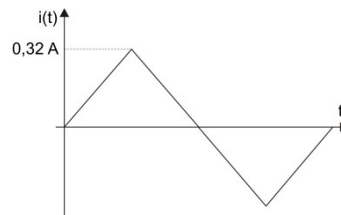


3.3. $\hat{i} = 1,12 \text{ A}$


3.4. $\hat{i} = 2,88 \text{ A}$

Aufgabe 4:

4.1.

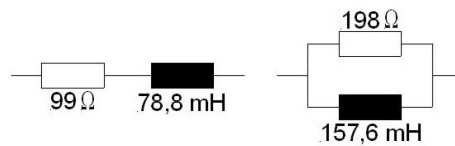

4.2.

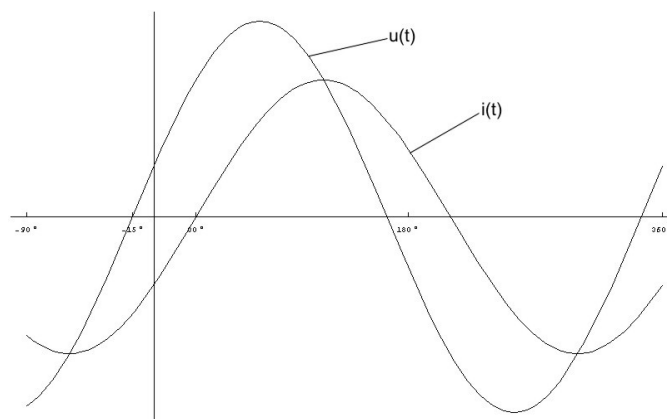


Reihenschaltung:

$$\hat{I} = 0,5 \text{ A} \cdot e^{-j30^\circ}$$

$$\hat{U}_R = 49,5 \text{ V} \cdot e^{-j30^\circ}$$
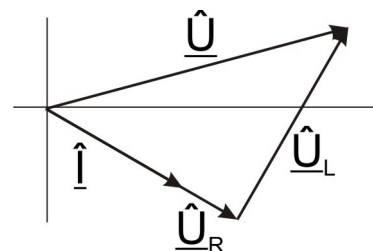
$$\hat{U}_L = 49,5 \text{ V} \cdot e^{j60^\circ}$$




Parallelschaltung:


$$\hat{U} = 70 \text{ V} \cdot e^{j15^\circ}$$

$$\hat{I}_R = 353,6 \text{ mA} \cdot e^{j15^\circ}$$

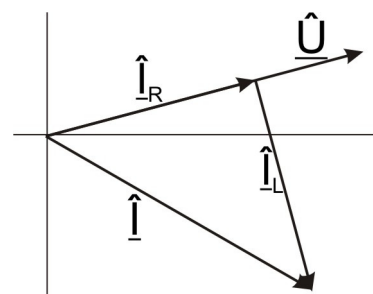
$$\hat{I}_L = 353,6 \text{ mA} \cdot e^{-j75^\circ}$$



4.3.1. $C_K = 4,02 \mu\text{F}$

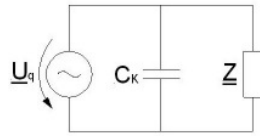

4.3.2. $C_K = 8,04 \mu\text{F}$

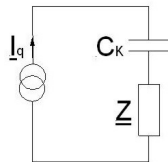

4.4.

